## ALTEC ENGINEERING NOTES

## TECHNICAL LETTER NO. 205

## HIGH-FREQUENCY DRIVER PROTECTION CAPACITOR FOR BIAMPLIFIED SOUND SYSTEMS

In sound systems which include biamplification, it is desirable to use a capacitor between the high-frequency amplifier and the 70V distribution system when conventional 70V line transformers are used.

> The capacitor isolation technique can be used at speaker impedances but this usually results in very large capacitance values.

The reason for the capacitor is to prevent low-frequency energy from the amplifier in reaching the driver (which may occur due turn on/turn off, line transients, etc.). Capacitive protection is not required if an ALTEC 15045A Line Transformer is used. A general rule would be to select a capacitor whose break point, with respect to the load impedance, would be 3 dB down at approximately one-half the high pass filter cutoff frequency of the biamplifier. Selection of power capacitance value can be easily determined from the graph in Figure 1. The lines on the graph represent the break point of the capacitor and load impedance. The following example is typical. The 50-watt tap of a 70V line distribution transformer has been selected. The biamplifier crossover frequency is 500 Hz. A line is drawn from the base of the graph at the 50W position and intersects the 300 Hz curve because the 300 Hz curve is approximately one-half the frequency break point. A horizontal line is drawn from the intersection of the vertical line and the 300 Hz line to the left side of the graph. The desired capacitance value is read at the left side of the graph. This value would be 5 microfarads.

The capacitors used for this application should be Mylar\* types but if electrolytic capacitors are used, they should be nonpolar.

> Paul Spranger Vice President Engineering

\*Mylar is a registered trademark of Dupont.



Figure 1. Protective Capacitance in Microfarads Versus Load in Watts

